
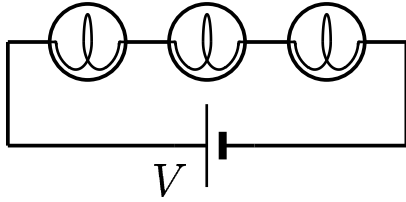


Three identical bulbs are connected in two ways as shown.

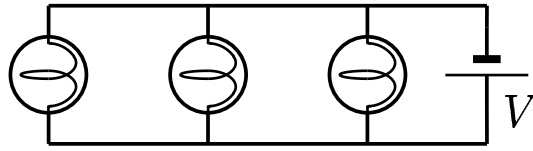

CASE I



CASE II

Determine $\frac{P_{\text{II}}}{P_{\text{I}}}$, where P_{I} is the power per bulb in CASE I, and P_{II} is in CASE II.

- A) $\frac{P_{\text{II}}}{P_{\text{I}}} = 9$
- B) $\frac{P_{\text{II}}}{P_{\text{I}}} = 3$
- C) $\frac{P_{\text{II}}}{P_{\text{I}}} = \frac{1}{3}$
- D) $\frac{P_{\text{II}}}{P_{\text{I}}} = \frac{1}{9}$

$$\frac{P_{\text{II}}}{P_{\text{I}}} = \frac{\frac{V^2}{R}}{\frac{(V/3)^2}{R}} = 9$$

Answer **A**.

27.06-01 Power in Two Circuits 2004-3-24