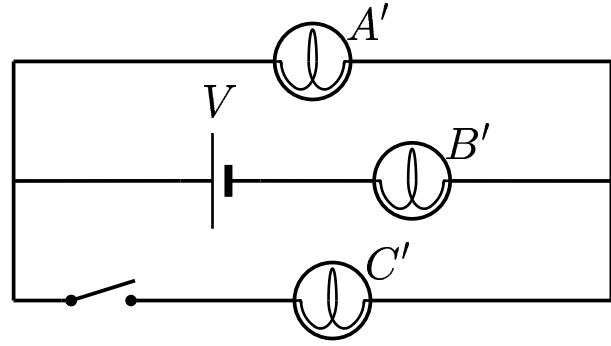
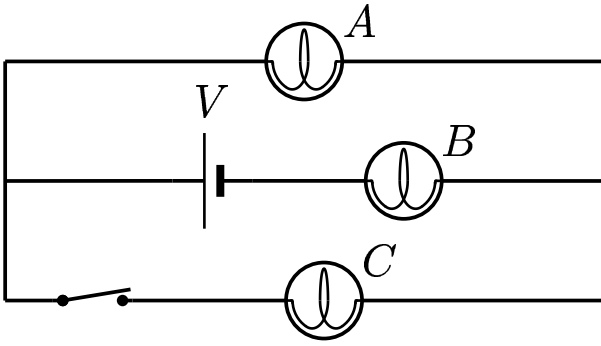


Three identical bulbs are connected in two ways as shown. Denote the brightness without a prime when the switch is closed and with a prime $'$ when the switch is open.



Compare the respective brightnesses of bulbs A and B when the switch is closed to when the switch is open.

- A) $B' > B$ and $A' > A$
- B) $B' < B$ and $A' > A$
- C) $B' > B$ and $A' < A$
- C) $B' < B$ and $A' < A$

$$\frac{I'_B}{I_B} = \frac{\frac{V}{2R}}{\frac{V}{\frac{3R}{2}}} = \frac{3}{4}$$

$$\frac{I'_A}{I_A} = \frac{\frac{V}{2R}}{\frac{1}{2} \frac{V}{\frac{3R}{2}}} = \frac{3}{2}$$

Since the brightness is directly proportional to the power $P = I^2 R$,
 $B' < B$ and $A' > A$.

Answer **B**.

28.02-06 Series and Parallel Circuits 2004-3-24