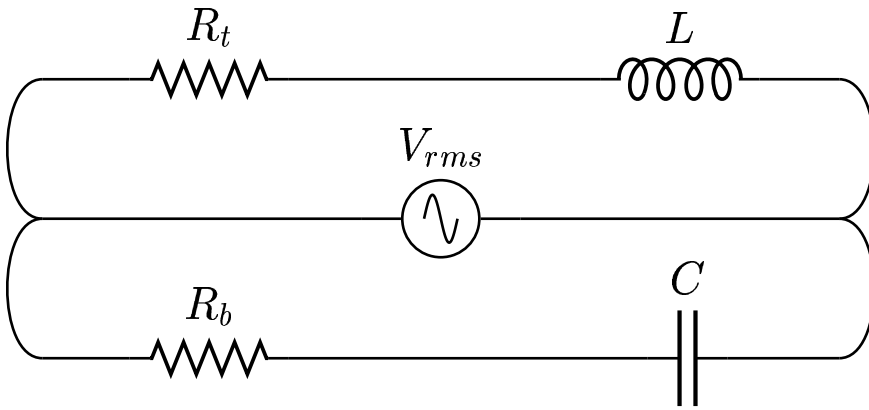


In the figure shown, the capacitance is  $C$  and the inductance is  $L$ . The resistance in the top branch is  $R_t$ , and in the bottom branch is  $R_b$ . The potential of the power supply is  $V_{rms}$ .



Find the rms current delivered by the power supply when the frequency is very small.

A)  $I = \frac{V_{rms}}{R_t + R_b}$

B)  $I = \frac{V_{rms}}{R_t}$

C)  $I = \frac{V_{rms}}{R_b}$

D)  $I = \frac{V_{rms} (R_t + R_b)}{R_t R_b}$

The impedance of the bottom and top branches is

$$Z_b = \sqrt{R_b^2 + \left(\frac{1}{\omega C}\right)^2} \quad \text{and} \quad Z_t = \sqrt{R_t^2 + (\omega L)^2}.$$

We notice that, when the frequency is very small,  $\frac{1}{\omega C} \rightarrow \infty$  and  $\omega L \rightarrow 0$ .

This means that the bottom branch, with very large impedance, carries negligible current; while the impedance of the top branch reduces to  $R_t$ . The current that flows in the power supply and the top branch is

$$I = I_t = \frac{V_{rms}}{Z_t} = \frac{V_{rms}}{R_t}.$$

Answer **B**.

33.01-02·RMS·Currents 2006-9-14