
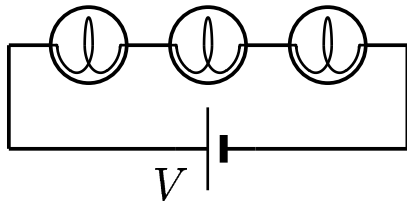


Three identical bulbs are connected in two ways as shown.

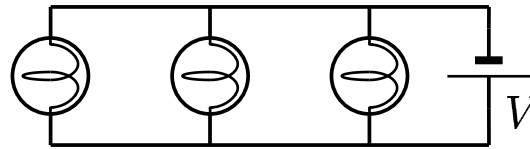

CASE I



CASE II

Determine  $\frac{P_{\text{II}}}{P_{\text{I}}}$ , where  $P_{\text{I}}$  is the power per bulb in CASE I, and  $P_{\text{II}}$  is in CASE II.

- A)  $\frac{P_{\text{II}}}{P_{\text{I}}} = 9$
- B)  $\frac{P_{\text{II}}}{P_{\text{I}}} = 3$
- C)  $\frac{P_{\text{II}}}{P_{\text{I}}} = \frac{1}{3}$
- D)  $\frac{P_{\text{II}}}{P_{\text{I}}} = \frac{1}{9}$

---

$$\frac{P_{\text{II}}}{P_{\text{I}}} = \frac{\frac{V^2}{R}}{\frac{(V/3)^2}{R}} = 9$$

Answer **A**.