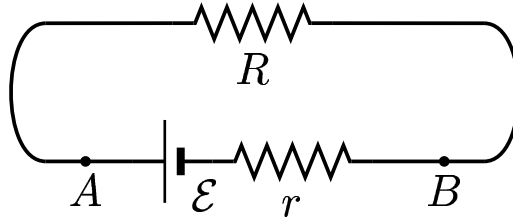


Given battery has *emf*  $\mathcal{E} = 10 \text{ V}$  and the internal resistance  $r = 1 \Omega$ , as shown in the figure below. An external resistance  $R = 0.01 \Omega$  is connected to the battery.



Compare  $V_{AB}$  with  $\mathcal{E}$ .

- A)  $V_{AB} \ll \mathcal{E}$ .
- B)  $V_{AB} \approx \mathcal{E}$ .
- C)  $V_{AB} \gg \mathcal{E}$ .

$$R_{total} = R + r$$

$$I = \frac{\mathcal{E}}{R + r}$$

$$V_{AB} = \frac{R}{R + r} \mathcal{E} = \frac{0.01}{0.01 + 1} 10 \text{ V} = .099 \text{ V}$$

This simple calculation shows  $V_{AB} = .099 \text{ V} \ll \mathcal{E}$ . In other words, when  $r \gg R$ , most of the potential drop is across the internal resistance  $r$ .

Answer **A**.