



Find the loop equation for the loop  $ABCD A$ .

- A)  $\mathcal{E}_2 + i_2 R_2 - \mathcal{E}_1 + i_1 R_1 = 0$
  - B)  $\mathcal{E}_2 - i_2 R_2 + \mathcal{E}_1 - i_1 R_1 = 0$
  - C)  $\mathcal{E}_2 + i_2 R_2 - \mathcal{E}_1 - i_1 R_1 = 0$
  - D)  $\mathcal{E}_2 + i_2 R_2 + \mathcal{E}_1 - i_1 R_1 = 0$
  - E)  $\mathcal{E}_2 - i_2 R_2 - \mathcal{E}_1 + i_1 R_1 = 0$
- 

For loop  $ABCD A$ , we have  $\mathcal{E}_2 - i_2 R_2 - \mathcal{E}_1 + i_1 R_1 = 0$

Convention 1:  $\Delta V = V_B - V_A = +\mathcal{E}$

$\Delta V = V_B - V_A = -\mathcal{E}$

Convention 2:  $\Delta V = V_D - V_C = -i R$

$\Delta V = V_D - V_C = +i R$

Convention 3: Currents into a junction are positive and currents out of a junction are negative.

Answer **E**.