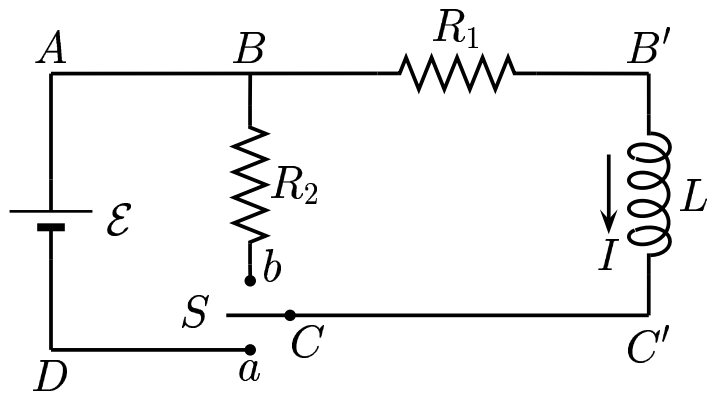


Consider the setup. Close S to the position “ a ” at $t = 0$.



Find I_∞ , i.e. the current flowing through L at a large t .

- A) $I_\infty = \frac{\mathcal{E}}{R_1}$.
- B) $I_\infty = \frac{\mathcal{E}}{R_2}$.
- C) $I_\infty = \mathcal{E} \left(\frac{1}{R_1} + \frac{1}{R_2} \right)$.
- D) $I_\infty = \mathcal{E} \left(\frac{1}{R_1 R_2} \right)$.

At large t , one expects that the current through L should reach a steady state. So the potential drop across L is 0. Here the inductor may be considered as a piece of wire. Therefore current through L is given by $\frac{\mathcal{E}}{R_1}$.

Answer **A**.