

Basic physics context of LC circuit.

Following is a more detailed version of an LC circuit. You may think of it as an expanded version of the 2 lines given in the summary page.

1. Basic equations.

Loop eqn: $V_L + V_C = 0$, where $V_L = L \frac{dI}{dt}$ and $V_C = \frac{q}{C}$. (1)

Energy: $U_L = \frac{1}{2} LI^2$, $U_C = \frac{1}{2C} q^2$. (2)

Power eqn: $P = \frac{dU}{dt} = \frac{d(qV)}{dt} = IV$

Power eqn = $I \times$ loop eqn = $IV_L + IV_C = 0$,

Or $0 = I \left(L \frac{dI}{dt} \right) + \frac{dq}{dt} \cdot \frac{q}{C} = \frac{d}{dt} \left[\frac{LI^2}{2} + \frac{q^2}{2C} \right] = \frac{d}{dt} (U_L + U_C)$ (3)

We will see LC circuit is analogous to the mass-spring system in mechanics. Here U_L and U_C is analogous to the kinetic energy (KE) and potential energy (PE) there.

For the mass-spring system conservation of energy implies during osc.

$(PE)_{max} = KE + PE = K_{max} = U_0$

For the LC circuit case, there are oscillations between U_L & U_C .

Correspondingly we have

$U_{Lmax} = U_L + U_C = U_{Cmax} = U_0$ (A)

2. Solutions to the LC loop eqn.

From eq(1) with $I = dQ/dt$, the loop eqn for q is

$$V_L + V_C = L \frac{dI}{dt} + \frac{q}{C} = L \frac{d^2q}{dt^2} + \frac{q}{C} = 0$$

Or $L \frac{d^2q}{dt^2} = -\frac{q}{C}$ (5)

In mechanics, you recall the mass-spring system satisfies the Hooke's Law, $F = ma$ implying that

$$m \frac{d^2x}{dt^2} = -kx$$

We can write it in the form: $\frac{d^2x}{dt^2} = -\omega^2 x$

The solution gives SHM, $x = x_{max} \cos(\omega t + \phi)$




where ϕ is the initial phase. For our illustration here, $\phi = 0$.

Analogous LC circuit solution is

$$q = q_{max} \cos \omega t \quad (6)$$

$$I = \frac{dq}{dt} = -\omega q_{max} \sin \omega t \equiv -I_{max} \sin \omega t \quad (7)$$

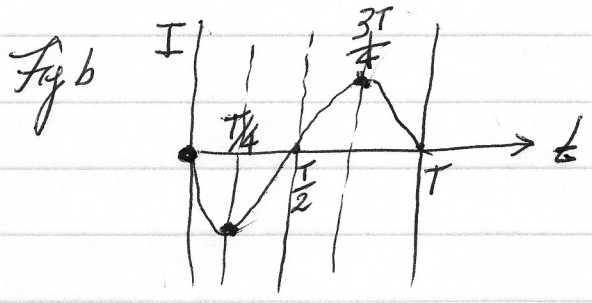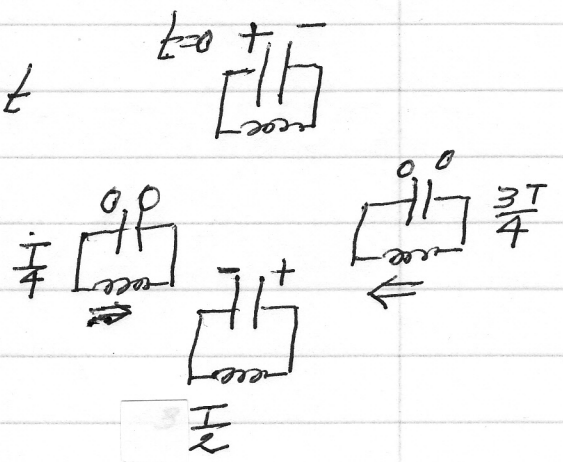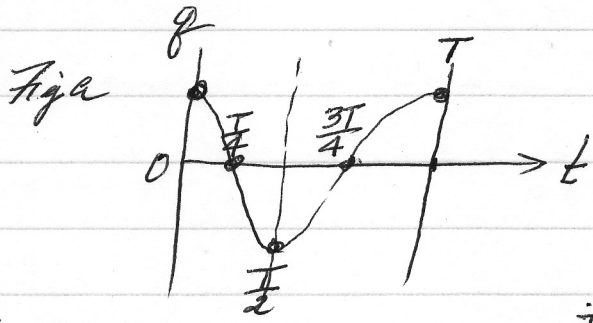Graphic illustration of the solution is shown in Fig a
+ Fig b.



Note: q is the charge on the left plate

The reader should step through the sequence

$$q = +q_{max}, 0, -q_{max}, 0, +q_{max}$$

for $t = 0, \frac{T}{4}, \frac{T}{2}, \frac{3T}{4}, T$.

2) For I , $I = -I_{max}$ at $\frac{T}{4}$ where q has max negative slope.

$I = +I_{max}$ at $\frac{3T}{4}$ where q has max. positive slope.

Also note that

$$U_L + U_C = \frac{1}{2} L (I_{max} \sin \omega t)^2 + \frac{1}{2} C (q_{max} \cos \omega t)^2$$

$$= \frac{1}{2} L I_{max}^2 (\sin^2 \omega t) + \frac{q_{max}^2}{2C} (\cos^2 \omega t) = U_0 (\sin^2 \omega t + \cos^2 \omega t) = U_0$$

where we have used: $\frac{1}{2} L I_{max}^2 = \frac{1}{2} L \omega^2 q_{max}^2 = \frac{1}{2} L \left(\frac{1}{LC}\right) q_{max}^2 = \frac{q_{max}^2}{2C} = U_0$